

## Lab #5 Practice Problem: Encoders and Decoders

Lecturer: Harikrishnan N B

Student:

## Background

### Decoders in System Design:

Decoders are fundamental building blocks in digital systems. By transforming compact binary inputs into one-hot outputs, they allow for easy comparison, selection, and condition checking. In this lab we explore their power in a real-world inspired “voting circuit” where decisions are made based on majority input values.

**One-hot** means that only one output/input line is active (logic 1) at a time, and all the other outputs/inputs are 0.

## Q1. Warm-up: Decoder Basics

1. Implement 2:4 decoder in `decoder_2to4.v` which takes two inputs - `A[1:0]` and an enable signal `E` and produces an output `O[3:0]`. All the bits in the output will be 0 whenever `E = 0`.
2. Implement 3:8 decoder in `decoder_3to8.v` using 2:4 decoder modules. The module should take two inputs - `A[2:0]` and an enable signal `E` and produces an output `O[7:0]`. All the bits in the output will be 0 whenever `E = 0`.
3. Implement a full adder in `fullAdder.v` using a 3:8 decoder and two OR gates. The module should take the usual inputs and produce the usual outputs.
4. Test your decoder and full adder by creating appropriate testbenches and testing against a truth table.

## Q2. CC Lab Circular Roll-Call

During CC attendance, the TA writes down the roll numbers of the next 4 students entering the lab as a short list: `[S0, S1, S2, S3]`.

The prof wants to see if the roll numbers form part of a circular roll-call — where one student’s number is immediately followed by its next roll number in order, either going forward (clockwise) or backward (counter-clockwise) in the cycle  $0 \rightarrow 1 \rightarrow 2 \rightarrow 3 \rightarrow 0$ .

You are given:

- the **4** roll numbers in order.
- an **anchor** number to start watching for.
- and a **mode**: 0 means look for a forward step ( $\text{anchor}, \text{anchor} + 1 \bmod 4$ ), and 1 means look for a backward step ( $\text{anchor}, \text{anchor} - 1 \bmod 4$ )

Your task is to:

1. Scan all 4 adjacent pairs  $(S_0, S_1)$ ,  $(S_1, S_2)$ ,  $(S_2, S_3)$ ,  $(S_3, S_0)$  (wrapping around).
2. Detect the first pair that shows  $(\text{anchor}, \text{anchor} \pm 1)$  depending on the mode.
3. Report the index (0-3) of the pair's starting position, and the second roll number in that pair.

**I/O:**

**1. Inputs:**

- $S_0[1:0]$ ,  $S_1[1:0]$ ,  $S_2[1:0]$ ,  $S_3[1:0]$  — 2-bit roll numbers in order.
- $PAT[1:0]$  — the anchor roll number.
- $MODE$  — 0 = forward, 1 = backward.

**2. Outputs:**

- $MATCH[3:0]$  — bit  $i$  is 1 if window  $(S_i, S_{(i+1) \bmod 4})$  matches the target pair.
- $ANY$  — 1 if any match exists.
- $PAR$  — parity (XOR) of  $MATCH$  bits (odd=1).
- $FIRST[1:0]$  — start index of the match; 00 if none.
- $Y[1:0]$  — the second roll number of the matching pair; 00 if none.

**Extra Rules:**

- It is guaranteed that there are 0 or 1 matches (never more). So  $MATCH$  is either all zeros or one hot (only one bit is 1; the rest are 0).
- The second roll number must be 00 if no match exists.

**Constraints:**

- Structural only. Allowed: gate primitives (and, or, xor, xnor, not, nand, nor, buf) and module instantiation.
- Forbidden: assign, always/initial, case/if, loops, equality/relational/arithmetic operators ( $=$ ,  $!=$ ,  $>$ ,  $<$ ,  $+$ ,  $-$ , etc.).
- Decoders/encoders are encouraged.

**Example 1:**

Input:  
 $S_0 = 2, S_1 = 3, S_2 = 1, S_3 = 0$   
 PAT = 2  
 MODE = 0

Output:  
 MATCH = 0001  
 ANY = 1  
 PAR = 1  
 FIRST = 00  
 Y = 3

1. **Work out the target pair** Since PAT = 2 and MODE = 0 (which means clockwise), the target pair we are looking for is: (2,3) because in a clockwise roll-call, the number after 2 should be 3.
2. **List all four adjacent pairs**  
 We now write down the four possible adjacent pairs of roll numbers from the array:
  - Pair starting at index 0  $\rightarrow (S_0, S_1) = (2, 3)$
  - Pair starting at index 1  $\rightarrow (S_1, S_2) = (3, 1)$
  - Pair starting at index 2  $\rightarrow (S_2, S_3) = (1, 0)$
  - Pair starting at index 3  $\rightarrow (S_3, S_0) = (0, 2)$  (note the wrap-around)
3. **Compare each pair to the target pair (2,3)**
  - The first pair (2,3) **matches** the target exactly.
  - The second pair (3,1) does not match because the first element is 3, not 2.
  - The third pair (1,0) does not match because the first element is 1, not 2.
  - The fourth pair (0,2) does not match because the first element is 0, not 2.
 So, only the pair starting at **index 0** is a match.
4. **Work out the outputs**
  - MATCH[3:0]: only the pair at index 0 matched, so this should be 0001.
  - ANY: since at least one match was found, ANY = 1.
  - PAR: there was exactly one match (an odd number), so PAR = 1.
  - FIRST: the first (and only) match was at index 0, so FIRST = 00.
  - Y: in the matching pair (2,3), the second roll number is 3. So Y = 3.

**Example 2:**

Input:  
 $S_0 = 1, S_1 = 0, S_2 = 3, S_3 = 2$   
 PAT = 2  
 MODE = 1

Output:  
 MATCH = 1000  
 ANY = 1  
 PAR = 1  
 FIRST = 11  
 Y = 1

**Q3. Circuit Design using Multiplexers (Optional Question for FUN)**

$$Z1 = ABC' + AB'C + A'BC$$

$$Z2 = AB + AC + BC$$

**Theory:**

1. Implement the functions using only three 2:1 multiplexers.

**Implementation:**

1. Implement 2:1 multiplexer in `mux_2to1.v`.
2. Implement your design in `mux_design.v`.
3. Verify outputs by creating a testbench and testing against a truth table.