


Shift Registers

Tutorial 7 - Digital Design (CS F215)


TAs - Ria Arora, Siddhant Kedia

What is a Register?

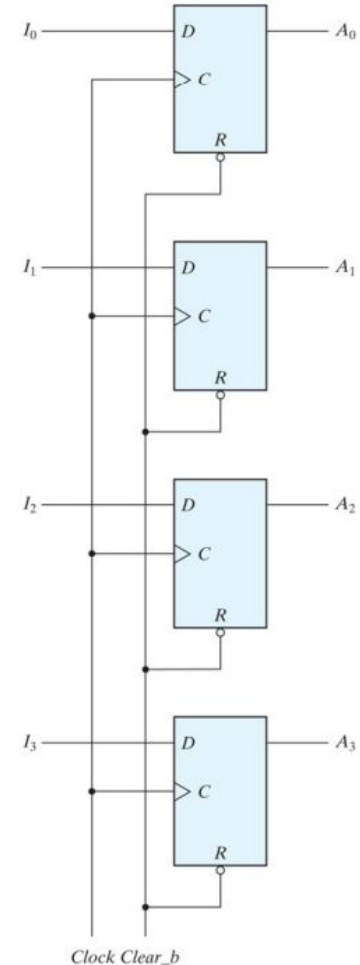
- A register is a group of flip-flops sharing a common clock.
- Each flip-flop in a register can store one bit of information.
- An n-bit register consists of a group of n flip-flops capable of storing n bits of binary information.



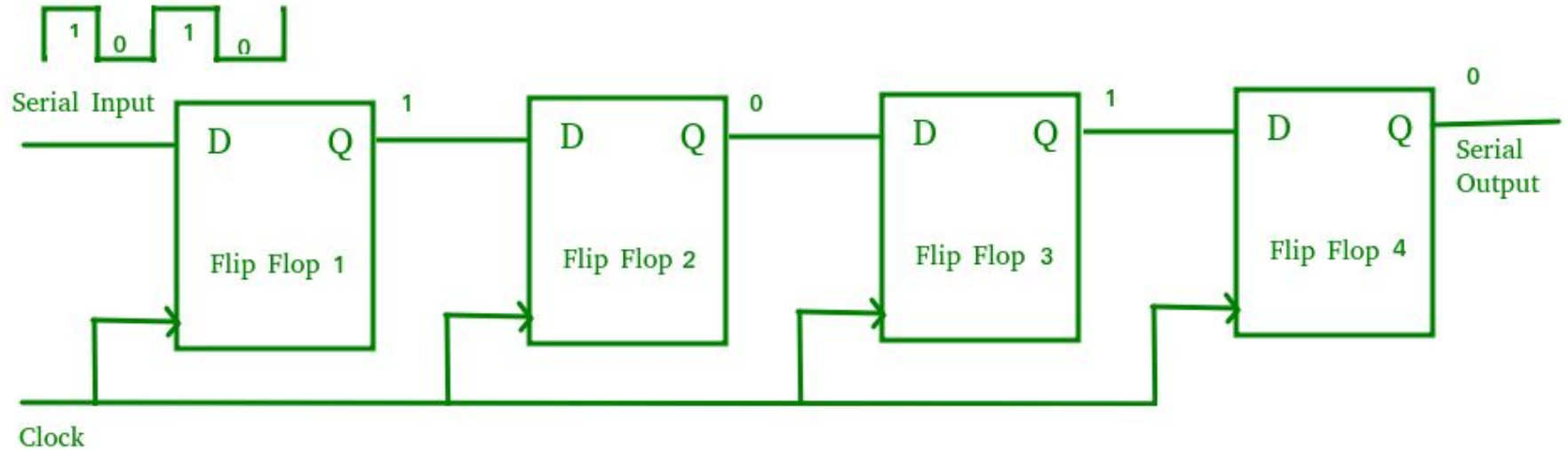
Serial-In Serial-Out Shift Register (SISO)



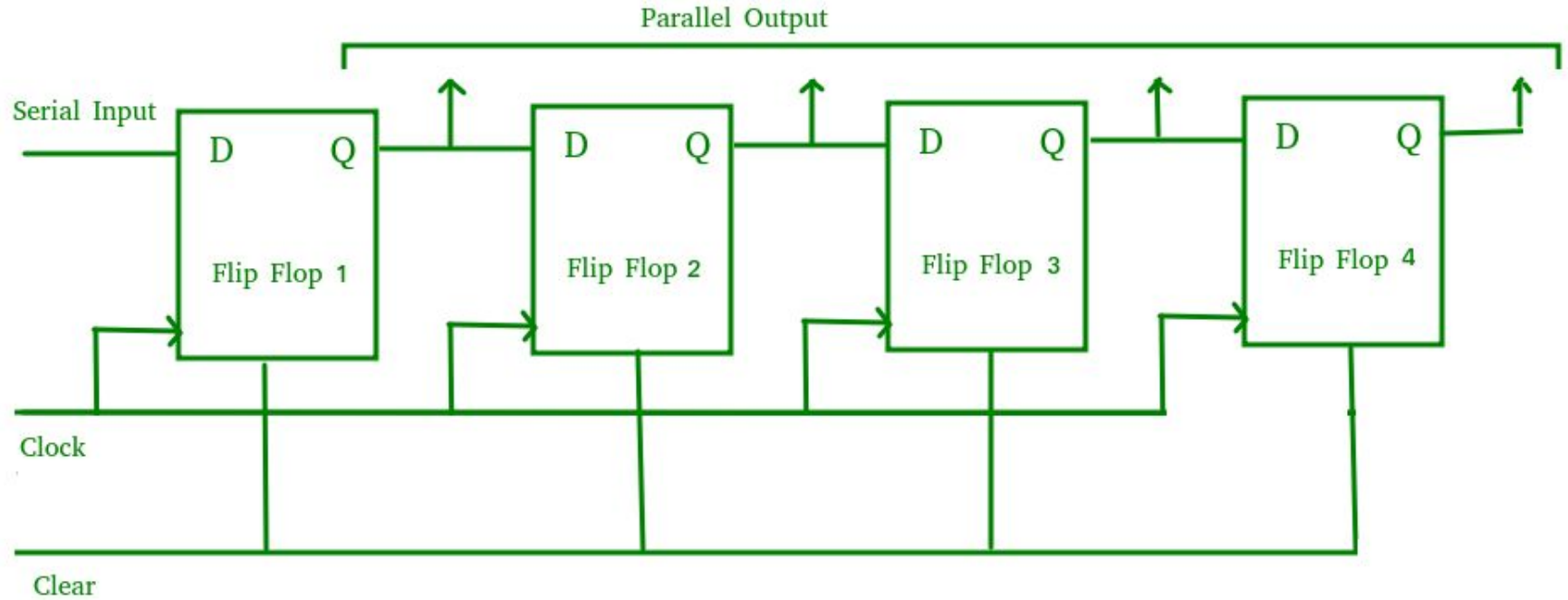
Serial-In Parallel-Out Shift Register (SIPO)



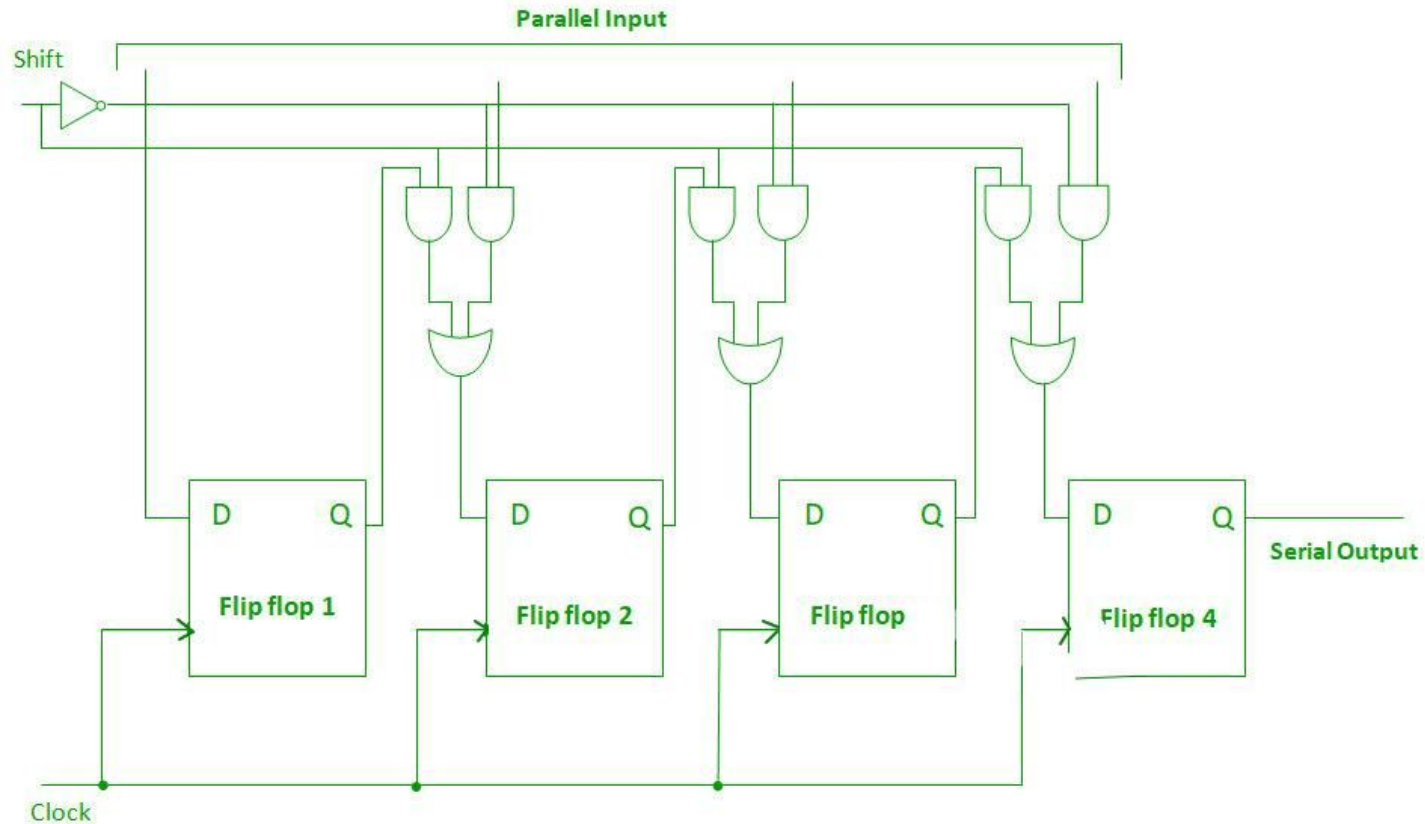Parallel-In Serial-Out Shift Register (PISO)



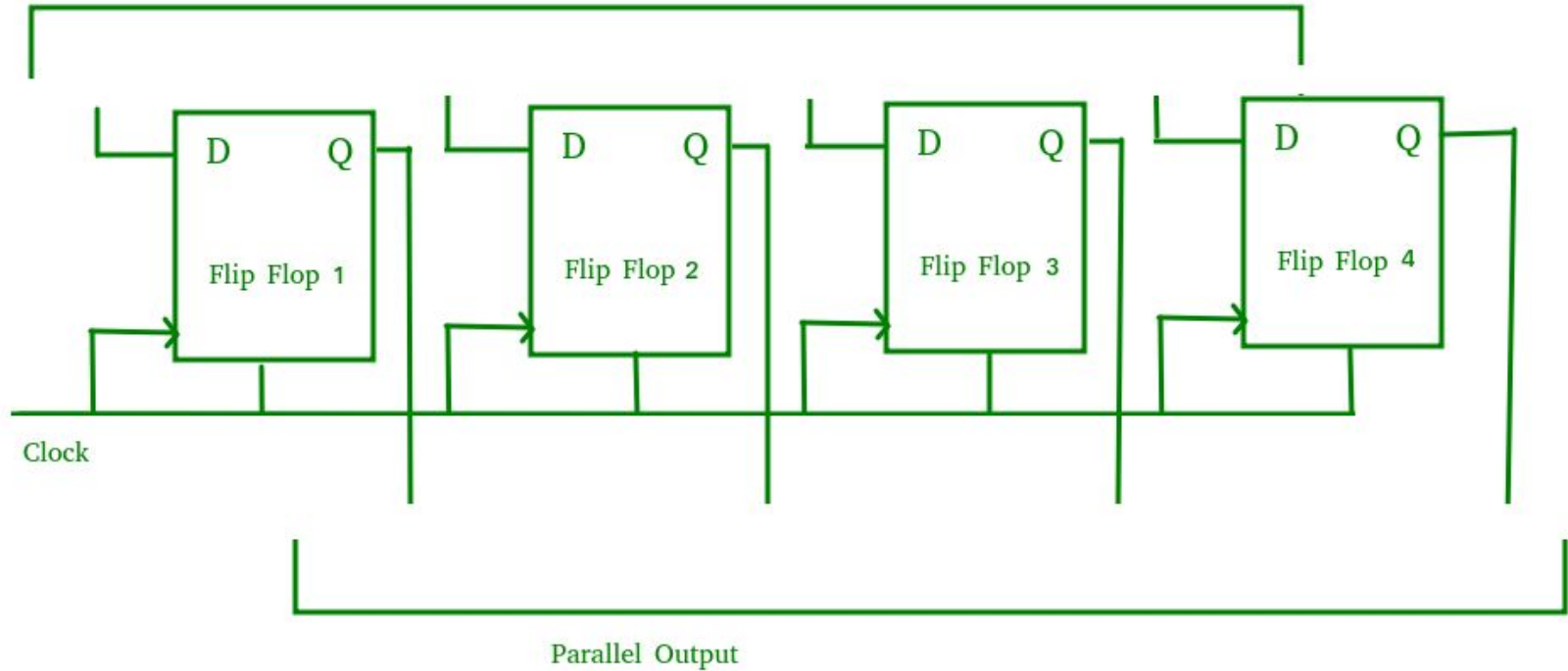Parallel-In Parallel-Out Shift Register (PIPO)



Q. Design a **pattern detector** that identifies the bit sequence **1011** from a serial input stream using a **shift register** and combinational logic.

1. **Shift Register Module:**

- Store the last 4 bits of a serial input.
- Shift left on each clock cycle and insert the new bit at LSB.

2. **Pattern Detector Module:**

- Read the shift register value.
- Output **1** when the pattern **1011** is detected, else **0**.

Note: The **top module** and **testbench** have already been implemented.

Example:

Input Bitstream: 1 0 1 1 0 1 1

Expected Detection Output: 0 0 0 1 0 0 1

- Each 1 in the output shows that 1011 was detected at that clock cycle.

Thank You